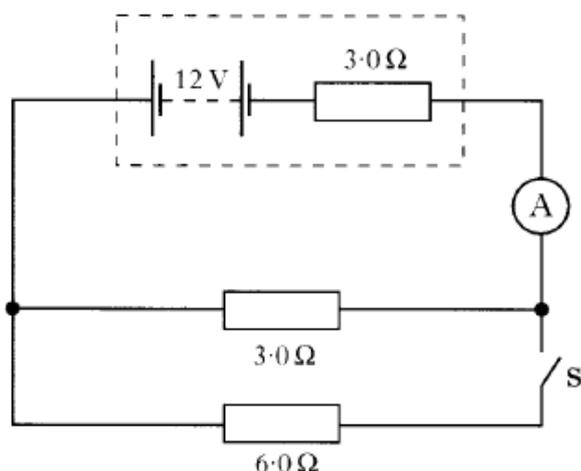


Exercise 12 - Emf and Internal Resistance

Past Paper Homework Questions


1. A battery of e.m.f. 12 V and internal resistance $3.0\ \Omega$ is connected in a circuit as shown.



When switch **S** is closed the ammeter reading changes from

- A 2.0 A to 1.0 A
 B 2.0 A to 2.4 A
 C 2.0 A to 10 A
 D 4.0 A to 1.3 A
 E 4.0 A to 6.0 A .
3. The e.m.f. of a battery is
- A the total energy supplied by the battery
 B the voltage lost due to the internal resistance of the battery
 C the total charge which passes through the battery
 D the number of coulombs of charge passing through the battery per second
 E the energy supplied to each coulomb of charge passing through the battery.

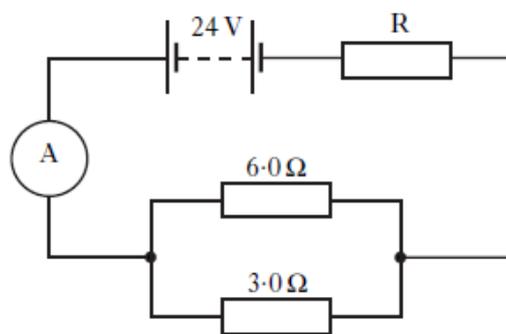
2. A battery of e.m.f. 24 V and negligible internal resistance is connected as shown.



The reading on the ammeter is 2.0 A .

The resistance of **R** is

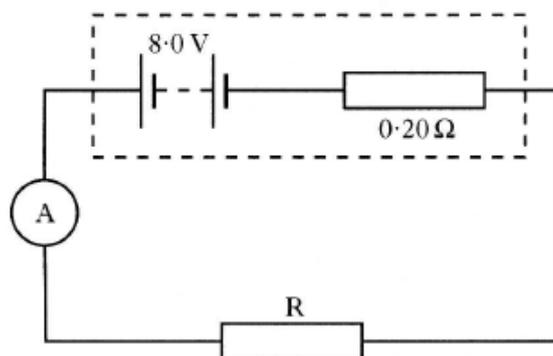- A $3.0\ \Omega$
 B $4.0\ \Omega$
 C $10\ \Omega$
 D $12\ \Omega$
 E $18\ \Omega$.
4. In the following circuit, the battery has an e.m.f. of 8.0 V and an internal resistance of $0.20\ \Omega$.




The reading on the ammeter is 4.0 A .

The resistance of **R** is


- A $0.5\ \Omega$
 B $1.8\ \Omega$
 C $2.0\ \Omega$
 D $2.2\ \Omega$
 E $6.4\ \Omega$.

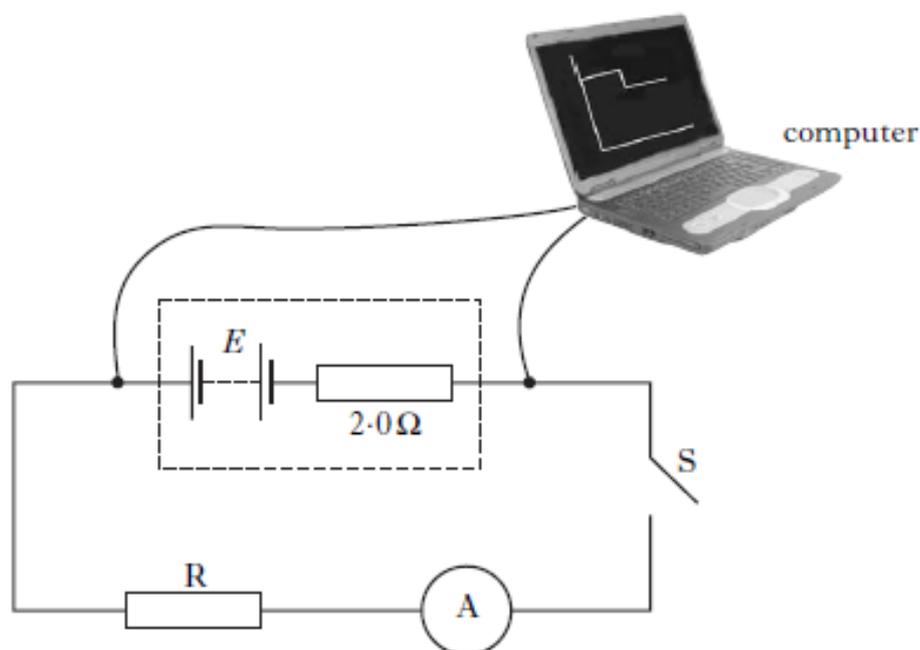5. A power supply of e.m.f. E and internal resistance $2.0\ \Omega$ is connected as shown.




The computer connected to the apparatus displays a graph of potential difference against time.

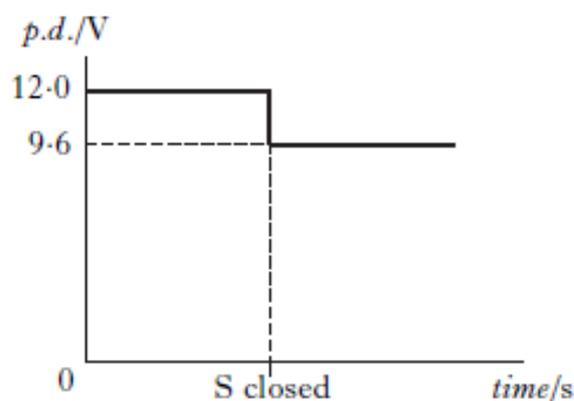The graph shows the potential difference across the terminals of the power supply for a short time before and after switch S is closed.



- (a) State the e.m.f. of the power supply. 1
- (b) Calculate:
- (i) the reading on the ammeter after switch S is closed; 2
- (ii) the resistance of resistor R . 1

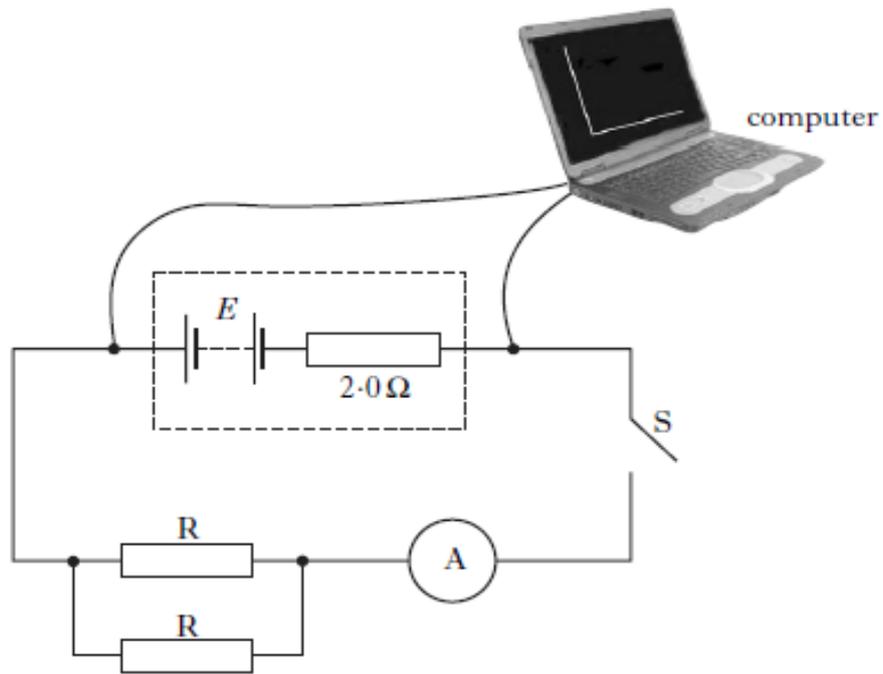- (c) Switch S is opened. A second identical resistor is now connected in parallel with R as shown.



The computer is again connected in order to display a graph of potential difference against time.




Copy and complete the new graph of potential difference against time showing the values of potential difference before and after switch S is closed.

6. Electrically heated gloves are used by skiers and climbers to provide extra warmth.



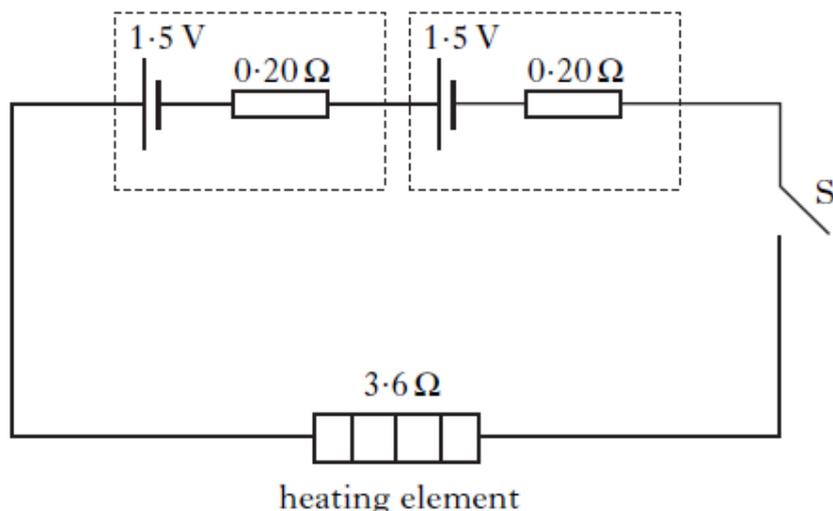- (a) Each glove has a heating element of resistance 3.6Ω .

Two cells, each of e.m.f. 1.5 V and internal resistance 0.20Ω , are used to operate the heating element.



Switch S is closed.

- | | |
|--|---|
| (i) Determine the value of the total circuit resistance. | 1 |
| (ii) Calculate the current in the heating element. | 2 |
| (iii) Calculate the power output of the heating element. | 2 |
- (b) When in use, the internal resistance of each cell gradually increases.
 What effect, if any, does this have on the power output of the heating element?
 Justify your answer.
- 2
(7)

7. (a) A supply of e.m.f. 10.0 V and internal resistance r is connected in a circuit as shown in Figure 1.

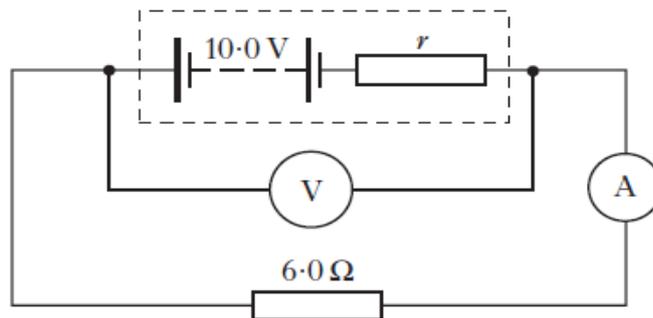


Figure 1

The meters display the following readings.

$$\text{Reading on ammeter} = 1.25\text{ A}$$

$$\text{Reading on voltmeter} = 7.50\text{ V}$$

- (i) What is meant by an *e.m.f. of 10.0 V* ? 1
- (ii) Show that the internal resistance, r , of the supply is $2.0\ \Omega$. 1
- (b) A resistor R is connected to the circuit as shown in Figure 2.

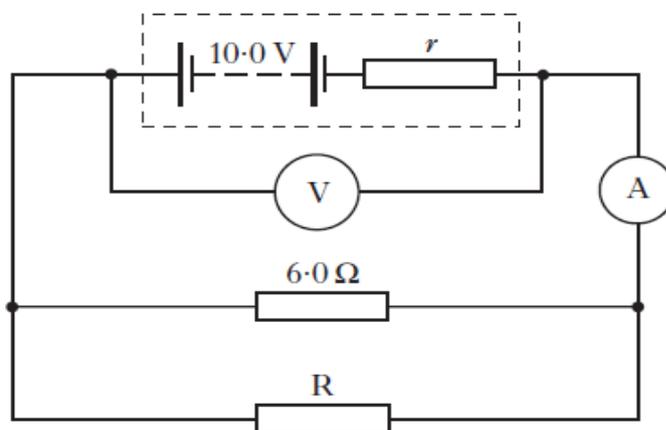


Figure 2


The meters now display the following readings.

$$\text{Reading on ammeter} = 2.0\text{ A}$$

$$\text{Reading on voltmeter} = 6.0\text{ V}$$


- (i) Explain why the reading on the voltmeter has decreased. 2
- (ii) Calculate the resistance of resistor R . 3
- (7)

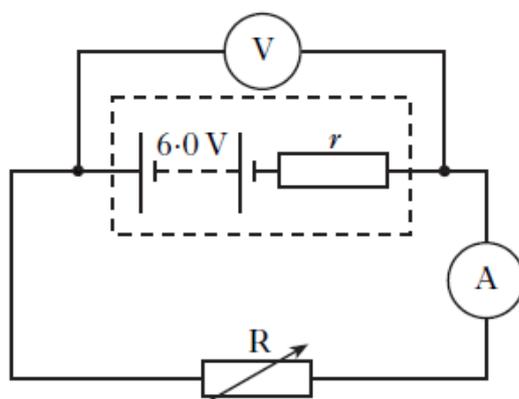8. A battery of e.m.f. 6.0 V and internal resistance, r , is connected to a variable resistor R as shown.



The graph shows how the current in the circuit changes as the resistance of R increases.

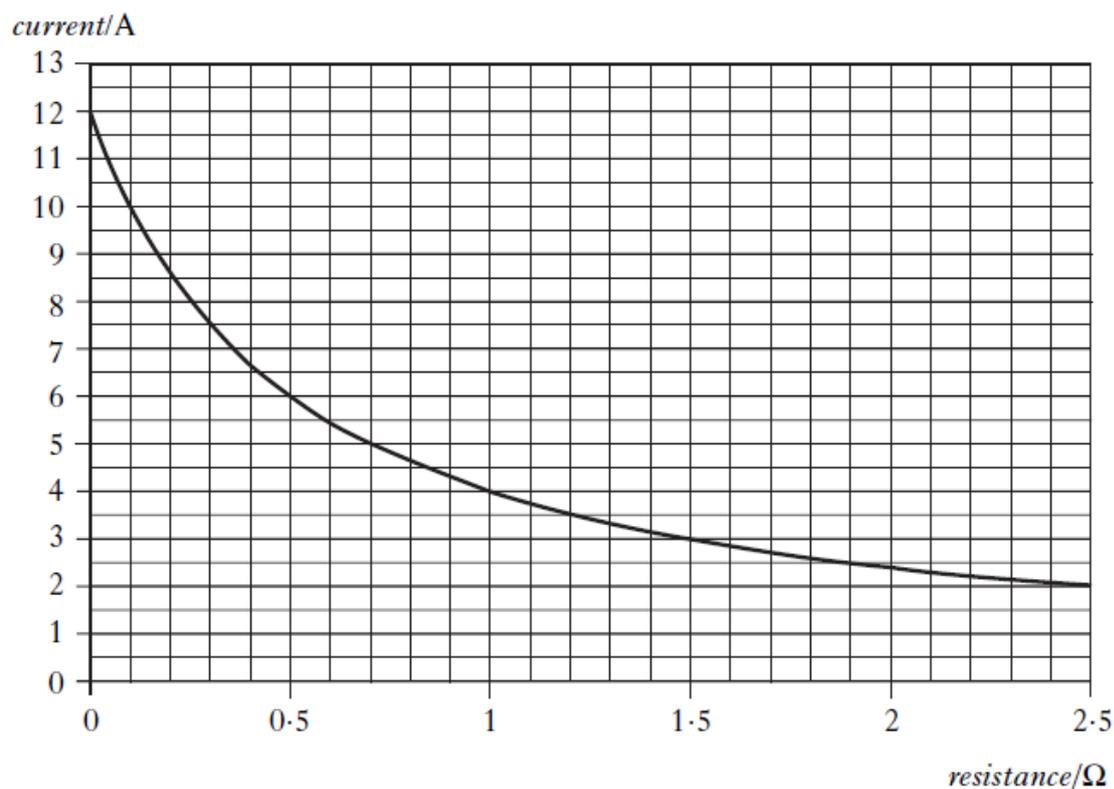The graph shows how the current in the circuit changes as the resistance of R increases.



- (a) Use information from the graph to calculate:
- the lost volts in the circuit when the resistance of R is $1.5\ \Omega$; 2
 - the internal resistance, r , of the battery. 2
- (b) The resistance of R is now increased.
 What effect, if any, does this have on the lost volts?
 You must justify your answer. 2